

Roll No.

Question Booklet Number

O. M. R. Serial No.

--	--	--	--	--	--	--	--

M. Sc. (Electronics) (Second Semester)
(NEP) EXAMINATION, 2025-26
ELECTRONIC CIRCUIT

Paper Code							
B	1	4	0	8	0	3	T

Questions Booklet
Series

B

Time : 1:30 Hours]

[Maximum Marks : 75

Instructions to the Examinee :

1. Do not open the booklet unless you are asked to do so.
2. The booklet contains 100 questions. Examinee is required to answer 75 questions in the OMR Answer-Sheet provided and not in the question booklet. All questions carry equal marks.
3. Examine the Booklet and the OMR Answer-Sheet very carefully before you proceed. Faulty question booklet due to missing or duplicate pages/questions or having any other discrepancy should be got immediately replaced.

परीक्षार्थियों के लिए निर्देश :

1. प्रश्न-पुस्तिका को तब तक न खोलें जब तक आपसे कहा न जाए।
2. प्रश्न-पुस्तिका में 100 प्रश्न हैं। परीक्षार्थी को 75 प्रश्नों को केवल दी गई OMR आन्सर-शीट पर ही हल करना है, प्रश्न-पुस्तिका पर नहीं। सभी प्रश्नों के अंक समान हैं।
3. प्रश्नों के उत्तर अंकित करने से पूर्व प्रश्न-पुस्तिका तथा OMR आन्सर-शीट को सावधानीपूर्वक देख लें। दोषपूर्ण प्रश्न-पुस्तिका जिसमें कुछ भाग छपने से छूट गए हों या प्रश्न एक से अधिक बार छप गए हों या उसमें किसी अन्य प्रकार की कमी हो, तो उसे तुरन्त बदल लें।

(Remaining instructions on the last page)

(शेष निर्देश अन्तिम पृष्ठ पर)

(Only for Rough Work)

1. Stability factor S should be :
 - (A) High
 - (B) Low
 - (C) Infinite
 - (D) Zero
2. Log amplifier uses :
 - (A) Diode
 - (B) Capacitor
 - (C) Inductor
 - (D) Transformer
3. Ideal op-amp has :
 - (A) Infinite bandwidth
 - (B) Zero gain
 - (C) High noise
 - (D) Low CMRR
4. Load regulation is :
 - (A) $\Delta V_{out}/\Delta V_{in}$
 - (B) $\Delta V_{out}/\Delta I_L$
 - (C) $\Delta V_{in}/\Delta I_L$
 - (D) $\Delta I_L/\Delta V_{in}$
5. Thermal runaway is reduced by :
 - (A) Increasing β
 - (B) Heat sink
 - (C) Increasing V_{in}
 - (D) Removing bias
6. f_β is :
 - (A) Unity gain frequency
 - (B) Cutoff frequency
 - (C) Oscillation frequency
 - (D) Ripple frequency
7. Level shifter changes :
 - (A) Frequency
 - (B) DC level
 - (C) Gain
 - (D) Phase
8. Transconductance multiplier outputs :
 - (A) Voltage
 - (B) Current
 - (C) Power
 - (D) Frequency

9. High frequency model includes :
- (A) Resistances only
 - (B) Capacitances
 - (C) Inductances
 - (D) Transformer
10. For sustained oscillation, total phase shift must be :
- (A) 180°
 - (B) 360°
 - (C) 90°
 - (D) 270°
11. An amplifier has gain $A = 200$. With negative feedback $\beta = 0.02$, closed-loop gain is :
- (A) 50
 - (B) 100
 - (C) 200
 - (D) 20
12. If loop gain $A\beta = 10$, bandwidth increases by factor :
- (A) 10
 - (B) 11
 - (C) $1/10$
 - (D) 9
13. Maximum efficiency of linear regulator is theoretically :
- (A) 50%
 - (B) 75%
 - (C) 100%
 - (D) V_{out}/V_{in}
14. A regulated power supply mainly consists of :
- (A) Transformer only
 - (B) Rectifier and filter only
 - (C) Rectifier, filter and regulator
 - (D) Oscillator
15. Schmitt trigger provides :
- (A) Amplification
 - (B) Hysteresis
 - (C) Integration
 - (D) Differentiation
16. Power amplifier operates near :
- (A) Cutoff
 - (B) Saturation
 - (C) Both (A) and (B)
 - (D) Active mid

17. Complementary symmetry uses :
- (A) NPN only
 - (B) PNP only
 - (C) NPN and PNP
 - (D) FET
18. Adder circuit sums :
- (A) Currents
 - (B) Voltages
 - (C) Power
 - (D) Frequency
19. At low frequencies gain reduces due to :
- (A) Capacitance
 - (B) Inductance
 - (C) Coupling capacitors
 - (D) β
20. Crossover distortion occurs in :
- (A) Class A
 - (B) Class B
 - (C) Class AB
 - (D) Class C
21. Wideband amplifier has :
- (A) Narrow BW
 - (B) Large BW
 - (C) No gain
 - (D) No cutoff
22. Input impedance of CE amplifier is :
- (A) High
 - (B) Low
 - (C) Infinite
 - (D) Zero
23. Efficiency of linear regulator is highest when :
- (A) $V_{in} \gg V_{out}$
 - (B) $V_{in} \approx V_{out}$
 - (C) $V_{out} \gg V_{in}$
 - (D) Ripple maximum
24. A Zener regulator has $V_Z = 6 \text{ V}$, $R_S = 200 \Omega$, $V_{in} = 12 \text{ V}$. Maximum load current without losing regulation is :
- (A) 10 mA
 - (B) 20 mA
 - (C) 30 mA
 - (D) 40 mA
25. Line regulation = 10 mV/V. If input changes by 5 V, output change is :
- (A) 5 mV
 - (B) 10 mV
 - (C) 50 mV
 - (D) 100 mV
26. Thermal stability is improved by :
- (A) Increasing I_c
 - (B) Increasing R_e
 - (C) Removing bias
 - (D) Increasing β

27. Input impedance of emitter follower is :
- (A) Low
 - (B) Very high
 - (C) Zero
 - (D) Unity
28. Output impedance of CE is :
- (A) High
 - (B) Low
 - (C) Zero
 - (D) Infinite
29. Oscillator requires :
- (A) External input
 - (B) DC supply
 - (C) Feedback
 - (D) All of the above
30. A Zener regulator : if load current increases, Zener current :
- (A) Increases
 - (B) Decreases
 - (C) Remains constant
 - (D) Becomes zero
31. Colpitts oscillator uses :
- (A) Split inductance
 - (B) Split capacitance
 - (C) RC network
 - (D) Transformer
32. An op-amp has open-loop gain = 10^5 . With $\beta = 0.01$, closed-loop gain is approximately :
- (A) 100
 - (B) 99
 - (C) 10^5
 - (D) 1000
33. Voltage to current converter uses :
- (A) Series feedback
 - (B) Shunt feedback
 - (C) No feedback
 - (D) Positive feedback
34. Main drawback of shunt regulator is :
- (A) High efficiency
 - (B) Poor regulation
 - (C) High power dissipation
 - (D) Complex design

35. In IC 723, error amplifier compares :
- (A) V_{in} and V_{out}
 - (B) V_{ref} and V_{out}
 - (C) V_{ref} and V_{in}
 - (D) I_L and V_{out}
36. Class A amplifier efficiency is (practical) :
- (A) 25%
 - (B) 50%
 - (C) 78.5%
 - (D) 100%
37. Bandwidth of op-amp increases with :
- (A) Gain
 - (B) Feedback
 - (C) Open loop
 - (D) Noise
38. h_{fe} represents :
- (A) Input impedance
 - (B) Current gain
 - (C) Voltage gain
 - (D) Output resistance
39. In transistor series regulator, pass transistor operates in :
- (A) Cutoff
 - (B) Saturation
 - (C) Active region
 - (D) Breakdown
40. High frequency cutoff occurs at is :
- (A) - 3 dB
 - (B) - 6 dB
 - (C) - 10 dB
 - (D) - 1 dB
41. Stability factor S for fixed bias is :
- (A) 1
 - (B) β
 - (C) $1 + \beta$
 - (D) 0
42. Hartley oscillator feedback element is :
- (A) RC
 - (B) LC
 - (C) Crystal
 - (D) Transformer

43. Lower cutoff frequency affected by :
- (A) Coupling capacitor
 - (B) R_C
 - (C) β
 - (D) V_{CC}
44. CE amplifier voltage gain formula :
- (A) $g_m R_C$
 - (B) R_C/g_m
 - (C) g_m/R_C
 - (D) βR_C
45. For ideal integrator, output is :
- (A) $-(1/RC) \int V_{in} dt$
 - (B) $(1/RC) dV_{in}/dt$
 - (C) $-RC dV_{in}/dt$
 - (D) V_{in}
46. Comparator works in :
- (A) Linear region
 - (B) Saturation
 - (C) Cutoff
 - (D) Active
47. Slew rate = 0.5 V/ μ s. Maximum frequency for 10 V peak sine wave is :
- (A) 8 kHz
 - (B) 80 kHz
 - (C) 800 kHz
 - (D) 1 kHz
48. Instrumentation amplifier's advantage is :
- (A) Low input impedance
 - (B) Low CMRR
 - (C) High input impedance and high CMRR
 - (D) Low gain
49. Load regulation formula is :
- (A) $\Delta V_{out}/\Delta V_{in}$
 - (B) $\Delta V_{out}/\Delta I_L$
 - (C) $\Delta V_{in}/\Delta I_L$
 - (D) $\Delta I_L/\Delta V_{in}$
50. h-parameter model is :
- (A) Large signal
 - (B) Small signal
 - (C) DC model
 - (D) Power model

51. Ideal op-amp output impedance :
- (A) Infinite
 - (B) High
 - (C) Low
 - (D) Zero
52. Zener diode works in :
- (A) Forward bias region
 - (B) Reverse breakdown region
 - (C) Cutoff region
 - (D) Saturation region
53. Emitter follower has voltage gain :
- (A) > 1
 - (B) $= 1$
 - (C) < 1 but ≈ 1
 - (D) 0
54. Ripple factor of full wave rectifier is approximately :
- (A) 1.21
 - (B) 0.482
 - (C) 0.707
 - (D) 0.318
55. Barkhausen criterion requires loop gain :
- (A) < 1
 - (B) > 1
 - (C) $= 1$
 - (D) 0
56. Inverting amplifier gain =
- (A) R_f/R_{in}
 - (B) $-R_f/R_{in}$
 - (C) R_{in}/R_f
 - (D) 1
57. Class C amplifier is used in :
- (A) Audio
 - (B) RF
 - (C) DC
 - (D) Power supply
58. Line regulation is defined as change in output voltage due to :
- (A) Change in load current
 - (B) Change in input voltage
 - (C) Change in temperature
 - (D) Change in frequency
59. Current gain of CE amplifier is :
- (A) 1
 - (B) β
 - (C) α
 - (D) 0
60. Output impedance of ideal regulator is :
- (A) High
 - (B) Infinite
 - (C) Zero
 - (D) Unity

61. IC 723 contains :
- (A) Rectifier
 - (B) Reference voltage source
 - (C) Transformer
 - (D) Oscillator
62. Negative feedback reduces :
- (A) Gain
 - (B) Bandwidth
 - (C) Stability
 - (D) Input impedance
63. Lower cutoff frequency depends on :
- (A) Coupling capacitor
 - (B) R_C
 - (C) β
 - (D) V_{CC}
64. Phase shift of CE amplifier is :
- (A) 0°
 - (B) 90°
 - (C) 180°
 - (D) 360°
65. Zener regulator is suitable for :
- (A) High power applications
 - (B) Low current applications
 - (C) AC regulation
 - (D) Oscillation
66. Loop gain =
- (A) $A\beta$
 - (B) A/β
 - (C) β/A
 - (D) $A + \beta$
67. Instrumentation amplifier has :
- (A) Low CMRR
 - (B) High CMRR
 - (C) Low input Z
 - (D) High output Z
68. Crystal oscillator frequency stability is :
- (A) Poor
 - (B) Moderate
 - (C) Excellent
 - (D) Low

69. Direct coupling passes :
- (A) AC only
 - (B) DC only
 - (C) AC and DC
 - (D) None of the above
70. In series regulator, power dissipation equals :
- (A) $V_{out} \times I_L$
 - (B) $(V_{in} - V_{out}) \times I_L$
 - (C) $V_{in} \times I_L$
 - (D) V_{in}/V_{out}
71. Self-bias uses :
- (A) Collector feedback
 - (B) Voltage divider
 - (C) Fixed bias
 - (D) No resistor
72. Comparator output is :
- (A) Linear
 - (B) Analog
 - (C) Digital
 - (D) Zero
73. Miller effect increases :
- (A) Input capacitance
 - (B) Output capacitance
 - (C) Gain
 - (D) Current
74. Class A amplifier efficiency max :
- (A) 25%
 - (B) 50%
 - (C) 78.5%
 - (D) 100%
75. In a Zener shunt regulator, regulation improves when :
- (A) Series resistance decreases
 - (B) Zener dynamic resistance increases
 - (C) Zener dynamic resistance decreases
 - (D) Load resistance decreases
76. Transconductance g_m equals :
- (A) I_C/V_T
 - (B) V_T/I_C
 - (C) β/I_C
 - (D) $I_C\beta$

77. High frequency cutoff is when gain falls by :
- (A) 50%
 - (B) 70.7%
 - (C) 3 dB
 - (D) 6 dB
78. Hartley oscillator uses :
- (A) RC
 - (B) LC
 - (C) Crystal
 - (D) Transformer
79. CMRR =
- (A) A_d/A_c
 - (B) A_c/A_d
 - (C) $A_d \times A_c$
 - (D) 1
80. Closed loop gain depends on :
- (A) Internal gain
 - (B) Feedback network
 - (C) Supply voltage
 - (D) Frequency only
81. Slew rate limits :
- (A) DC gain
 - (B) Max frequency
 - (C) Max rate of change
 - (D) Input impedance
82. Stability factor for fixed bias is :
- (A) 1
 - (B) β
 - (C) $1 + \beta$
 - (D) 0
83. Push pull reduces :
- (A) Even harmonics
 - (B) Odd harmonics
 - (C) Noise
 - (D) Gain
84. Band width of cascaded stages :
- (A) Increases
 - (B) Decreases
 - (C) Remains same
 - (D) Infinite

85. Precision rectifier eliminates :
- (A) Ripple
 - (B) Threshold drop
 - (C) Noise
 - (D) Gain
86. Peak inverse voltage of bridge rectifier diode is :
- (A) V_m
 - (B) $2V_m$
 - (C) $V_m/2$
 - (D) $4V_m$
87. Differential amplifier amplifies :
- (A) Common mode
 - (B) Difference
 - (C) Noise
 - (D) Power
88. Emitter resistance improves :
- (A) Gain
 - (B) Stability
 - (C) Noise
 - (D) Distortion
89. Wein bridge oscillator gives :
- (A) Square wave
 - (B) Sine wave
 - (C) Sawtooth
 - (D) Pulse
90. Open loop gain of op-amp is :
- (A) Low
 - (B) Moderate
 - (C) Very high
 - (D) Zero
91. Percentage regulation is minimum for :
- (A) Good regulator
 - (B) Poor regulator
 - (C) No regulator
 - (D) Half wave rectifier
92. Series regulator provides :
- (A) Better regulation than shunt
 - (B) Worse regulation
 - (C) Same regulation
 - (D) No regulation

93. RC oscillators are suitable for :
- (A) RF
 - (B) Audio
 - (C) Microwave
 - (D) DC
94. Voltage shunt feedback reduces :
- (A) Input impedance
 - (B) Output impedance
 - (C) Gain
 - (D) Distortion
95. Oscillation requires total phase shift :
- (A) 90°
 - (B) 180°
 - (C) 360°
 - (D) 270°
96. Q-point lies in :
- (A) Cutoff
 - (B) Saturation
 - (C) Active region
 - (D) Breakdown
97. Zener resistance in breakdown region is :
- (A) Very high
 - (B) Very low
 - (C) Infinite
 - (D) Zero
98. Current mirror provides :
- (A) Voltage source
 - (B) Current source
 - (C) Oscillation
 - (D) Feedback
99. Gain with feedback =
- (A) $A/(1 - A\beta)$
 - (B) $A/(1 + A\beta)$
 - (C) $A\beta$
 - (D) β/A
100. A CE amplifier has $g_m = 40 \text{ mS}$ and $R_C = 2 \text{ k}\Omega$. Voltage gain is approximately :
- (A) 40
 - (B) 80
 - (C) 100
 - (D) 160

(Only for Rough Work)

4. Four alternative answers are mentioned for each question as—A, B, C & D in the booklet. The candidate has to choose the correct answer and mark the same in the OMR Answer-Sheet as per the direction :

Example :

Question :

- Q. 1 (A) ● (C) (D)
 Q. 2 (A) (B) ● (D)
 Q. 3 (A) ● (C) (D)

Illegible answers with cutting and over-writing or half filled circle will be cancelled.

5. Each question carries equal marks. Marks will be awarded according to the number of correct answers you have.
6. All answers are to be given on OMR Answer Sheet only. Answers given anywhere other than the place specified in the answer sheet will not be considered valid.
7. Before writing anything on the OMR Answer Sheet, all the instructions given in it should be read carefully.
8. After the completion of the examination candidates should leave the examination hall only after providing their OMR Answer Sheet to the invigilator. Candidate can carry their Question Booklet.
9. There will be no negative marking.
10. Rough work, if any, should be done on the blank pages provided for the purpose in the booklet.
11. To bring and use of log-book, calculator, pager and cellular phone in examination hall is prohibited.
12. In case of any difference found in English and Hindi version of the question, the English version of the question will be held authentic.

Impt. : On opening the question booklet, first check that all the pages of the question booklet are printed properly. If there is any discrepancy in the question Booklet, then after showing it to the invigilator, get another question Booklet of the same series.

4. प्रश्न-पुस्तिका में प्रत्येक प्रश्न के चार सम्भावित उत्तर—A, B, C एवं D हैं। परीक्षार्थी को उन चारों विकल्पों में से सही उत्तर छँटना है। उत्तर को OMR आन्सर-शीट में सम्बन्धित प्रश्न संख्या में निम्न प्रकार भरना है :

उदाहरण :

प्रश्न :

- प्रश्न 1 (A) ● (C) (D)
 प्रश्न 2 (A) (B) ● (D)
 प्रश्न 3 (A) ● (C) (D)

अपठनीय उत्तर या ऐसे उत्तर जिन्हें काटा या बदला गया है, या गोले में आधा भरकर दिया गया, उन्हें निरस्त कर दिया जाएगा।

5. प्रत्येक प्रश्न के अंक समान हैं। आपके जितने उत्तर सही होंगे, उन्हीं के अनुसार अंक प्रदान किये जायेंगे।
6. सभी उत्तर केवल ओ. एम. आर. उत्तर-पत्रक (OMR Answer Sheet) पर ही दिये जाने हैं। उत्तर-पत्रक में निर्धारित स्थान के अलावा अन्यत्र कहीं पर दिया गया उत्तर मान्य नहीं होगा।
7. ओ. एम. आर. उत्तर-पत्रक (OMR Answer Sheet) पर कुछ भी लिखने से पूर्व उसमें दिये गये सभी अनुदेशों को सावधानीपूर्वक पढ़ लिया जाये।
8. परीक्षा समाप्ति के उपरान्त परीक्षार्थी कक्ष निरीक्षक को अपनी OMR Answer Sheet उपलब्ध कराने के बाद ही परीक्षा कक्ष से प्रस्थान करें। परीक्षार्थी अपने साथ प्रश्न-पुस्तिका ले जा सकते हैं।
9. निगेटिव मार्किंग नहीं है।
10. कोई भी रफ कार्य, प्रश्न-पुस्तिका के अन्त में, रफ-कार्य के लिए दिए खाली पेज पर ही किया जाना चाहिए।
11. परीक्षा-कक्ष में लॉग-बुक, कैलकुलेटर, पेजर तथा सेल्युलर फोन ले जाना तथा उसका उपयोग करना वर्जित है।
12. प्रश्न के हिन्दी एवं अंग्रेजी रूपान्तरण में भिन्नता होने की दशा में प्रश्न का अंग्रेजी रूपान्तरण ही मान्य होगा।

महत्वपूर्ण : प्रश्नपुस्तिका खोलने पर प्रथमतः जाँच कर देख लें कि प्रश्न-पुस्तिका के सभी पृष्ठ भलीभाँति छपे हुए हैं। यदि प्रश्नपुस्तिका में कोई कमी हो, तो कक्षनिरीक्षक को दिखाकर उसी सिरीज की दूसरी प्रश्न-पुस्तिका प्राप्त कर लें।